

# EE213 Exam 1

March 12, 2014

Closed Book, Justify all work unless otherwise instructed.

Good Luck


NAME\_\_\_\_\_

student ID number \_\_\_\_\_

1	/25
2	/25
3	/25
4	/25
TOTAL	/100

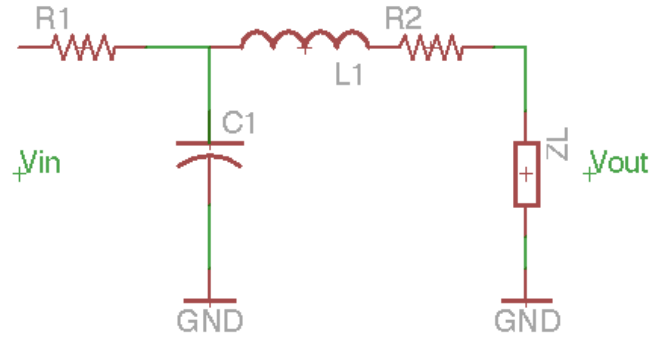1) (25) Consider the following circuit with  $R_1 = 10\Omega$ ,  $R_2 = 10\Omega$ ,  $C_1 = 10mF$ , and  $L_1 = 1H$ , and input voltage  $v_{in}(t) = 10\cos(10t)$ .

- Find the Thevenin equivalent circuit (Thevenin voltage and impedance, do not include  $Z_L$ ) for the circuit output  $v_{out}(t)$ .
- Determine the impedance  $Z_L$  at output  $v_{out}(t)$  that will result in maximal average power delivered to  $Z_L$ . Determine this maximum average power delivered to  $Z_L$ .




2) (25) Consider the circuit below.

a) Let  $R_3 = R_4$ . What is the voltage at the positive input of the opamp?


b) Assuming a), write two nodal equations by hand.

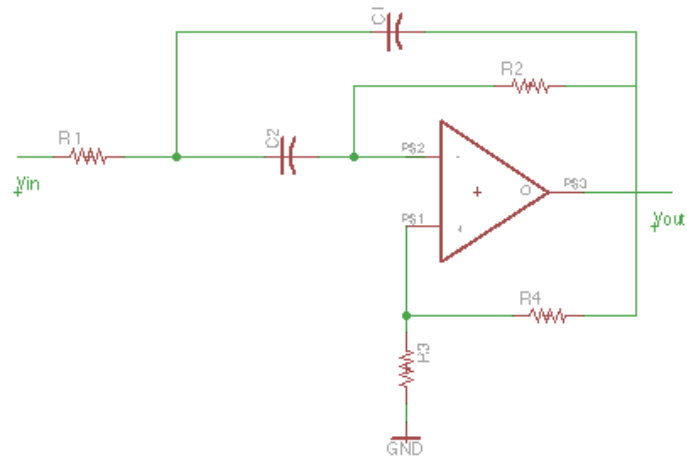c) From b) find the transfer function  $H(s) = V_{out}(s)/V_{in}(s)$  by hand.



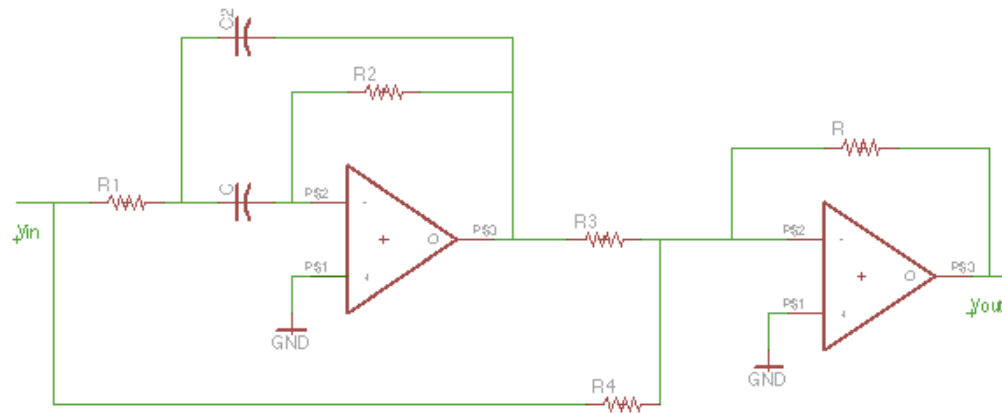3) (25) Consider the circuit below.

- Write MATLAB code to determine the transfer function  $H(s) = V_{OUT}(s)/V_{IN}(s)$ . Do not solve for the transfer function.
- Write matlab code to find the zero state response.
- Determine the value of the transfer function  $H(s)$  at very high and very low frequencies from physical arguments.



4) (25) Consider a circuit that has the following transfer function.

$$H(s) = \frac{2s + 3}{s + 4}$$

- a) Find the impulse response,  $h(t)$
- b) Find the step response  $s(t)$ .
- c) If the input to the circuit is  $x(t) = 10 \cos(2t - \pi/4)$ , find the output  $y(t)$  assuming the above transfer function.