
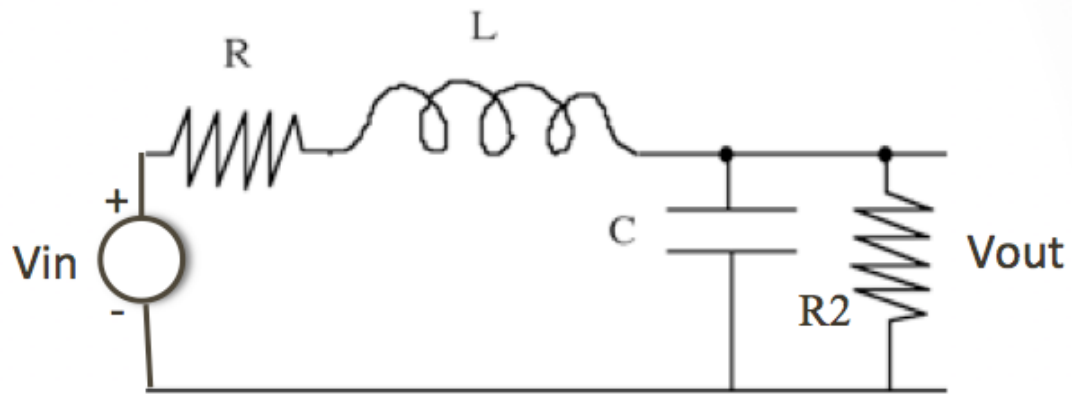


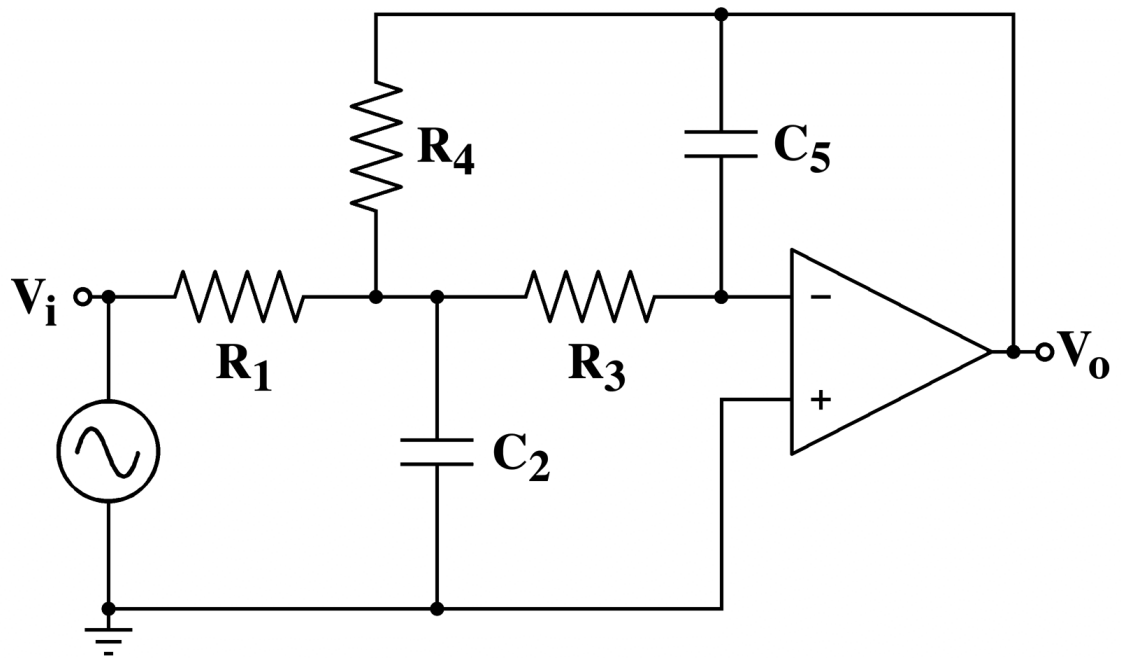
- 1) (25) Let $V_{in}(t) = 10 \cos(10t)$, $R = 10\Omega$, $L = 1H$, $C = 10mF$, and $R_2 = 10\Omega$.
- (a) Find the Thevenin equivalent circuit (Thevenin voltage and impedance) for the circuit output $v_{out}(t)$.
- (b) Determine the impedance Z_L at output $v_{out}(t)$ that will result in maximal average power delivered to Z_L . Determine this maximal average power delivered to Z_L .



- 2) (a) For the circuit below compute by hand (do not use matlab) the transfer function $H(s) = V_o(s)/V_i(s)$.
(b) Consider a step input use physical arguments to find the initial and final values of V_o .



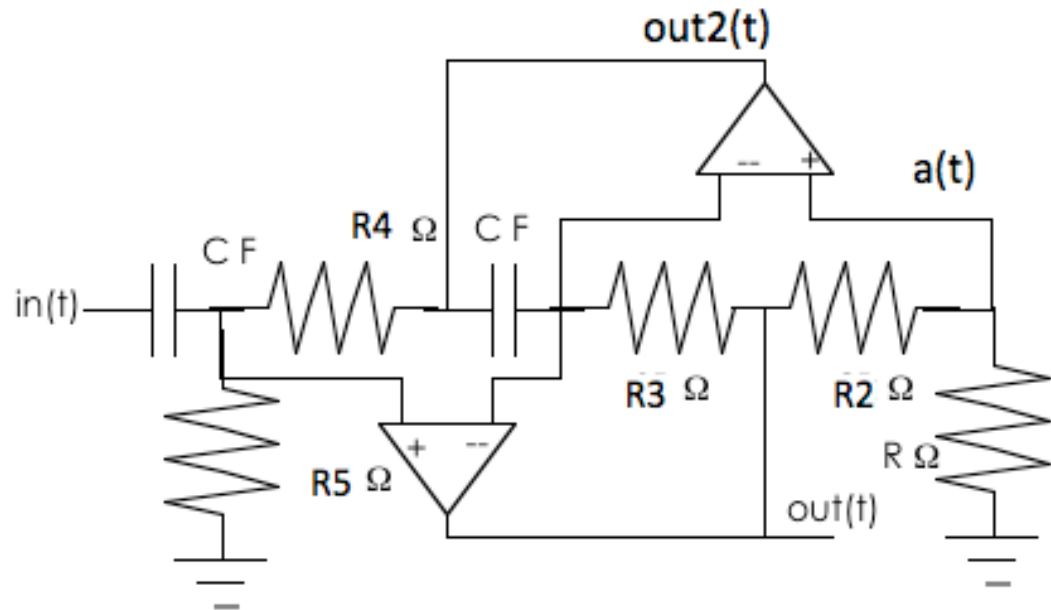- 3) (25) Use matlab to determine the transfer function $H(s) = \text{OUT}(s)/\text{IN}(s)$. Use matlab to find the step response for this transfer function.



- 4) (25) Consider the transfer function $H(s) = 1/(s^2 + 5s + 4)$.
- (a) Find the impulse response $h(t)$.
 - (b) Find the step response $s(t)$.
 - (c) If the input to the circuit is $x(t) = 10\cos(5t)$ and the transfer function is given as above find the output $y(t)$.