
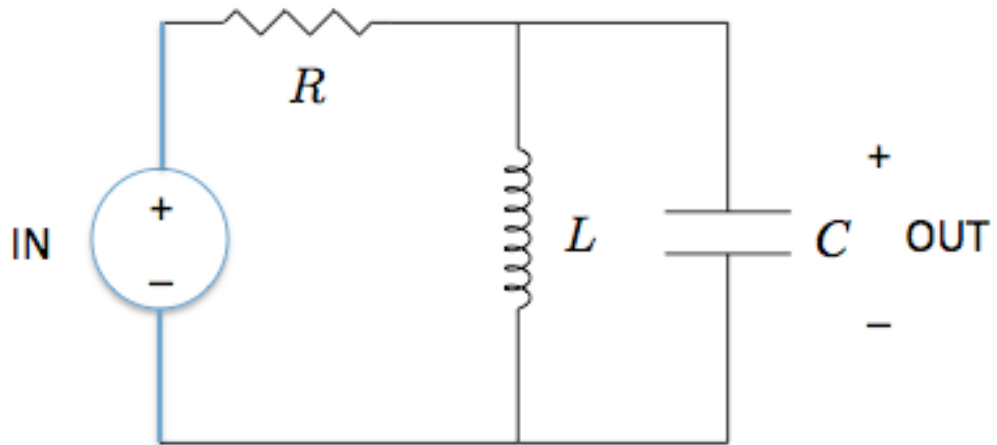


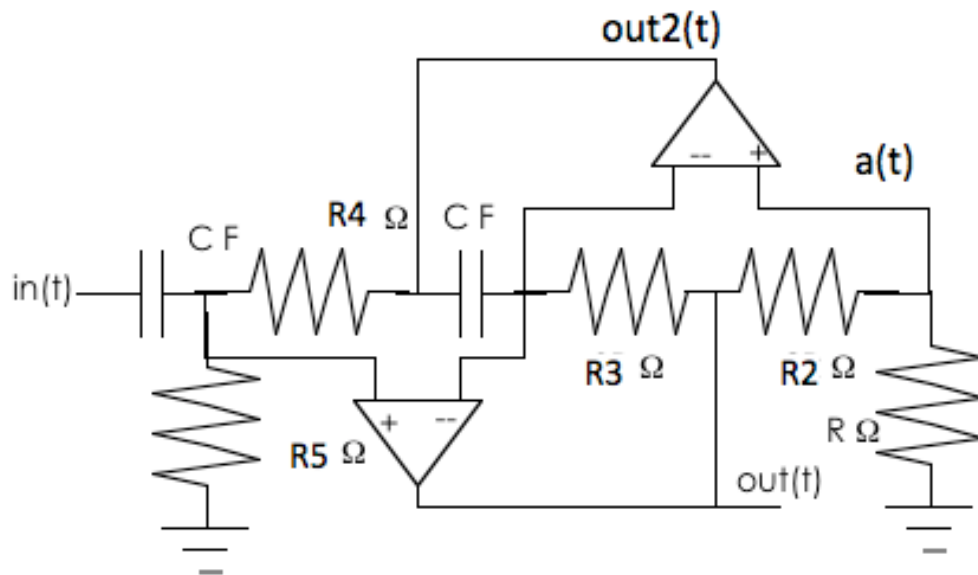- 1) The impulse response of a system is $h(t) = u(t) - u(t-4)$.
- If the input to the system is given by $x(t) = \exp(-t) u(t)$, find the output $y(t)$.
 - Find the natural response of the system given by $n(t)$.
- 2) Consider the circuit below where $R=5\Omega$, $L = 4\text{H}$, and $C = 0.05\text{F}$.
- Find the transfer function $H(s) = \text{OUT}(s)/\text{IN}(s)$ and the impulse response $h(t)$.
 - Find the zero input response at $\text{out}(t)$ when the inductor has an initial current from top to bottom; $i_L(0) = 0.1\text{A}$. There is zero initial charge on the capacitor.



- 3) Consider the circuit below. The output is given by $\text{out}(t)$. Find the state and then determine the state space representation.



- 4) A circuit is described by the following differential equation where $y(t)$ is the output and $in(t)$ is the input .


$$d^2y(t)/dt^2 + 5dy(t)/dt + y(t) = 2 \, din(t)/dt + in(t)$$

- (a) Find the transfer function for this circuit.
 - (b) Write a Matlab script to express the transfer function in symbolic form and from this find the poles of the system.
 - (c) Write a Matlab script to find the state space realization from the transfer function.
 - (d) Write a Matlab script to find the total response when $x(0) = [1 \, -1]'$ and $in(t) = \exp(-t) \cos(2t) u(t)$.
- 1) The impulse response of a system is $h(t) = u(t) - u(t-2)$.
- c) If the input to the system is given by $x(t) = \exp(-2t) u(t)$, find the output $y(t)$.
 - d) Find the natural response of the system given by $n(t)$.


2) Consider the circuit below where $R=10/3\Omega$, $L = 5H$, and $C = 0.1F$.

a) Find the transfer function $H(s) = OUT(s)/IN(s)$ and the impulse response $h(t)$.

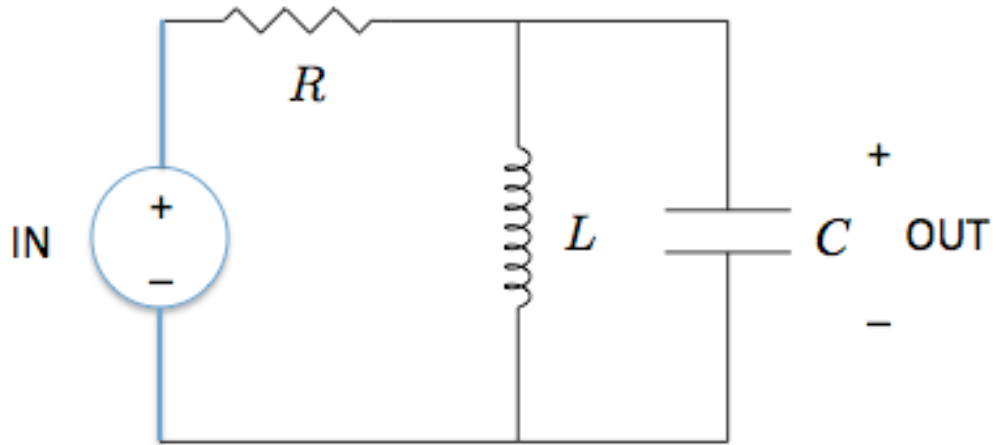b) Find the zero input response at $out(t)$ when the inductor has an initial current from top to bottom; $i_L(0) = 0.1A$. There is zero initial charge on the capacitor.



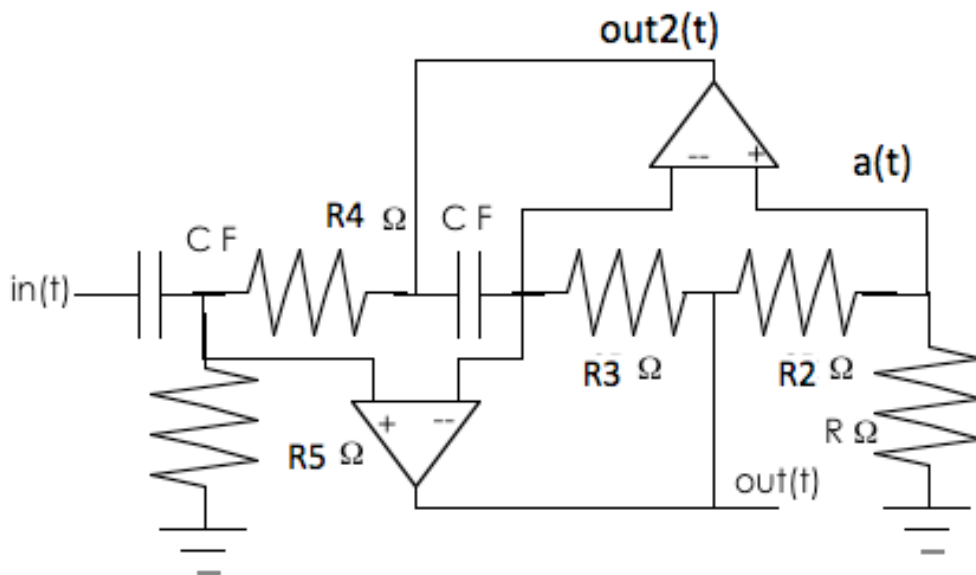3) Consider the circuit below. The output is given by $out2(t)$. Find the state and then determine the state space representation.



4) A circuit is described by the following differential equation where $y(t)$ is the output and $in(t)$ is the input .

$$d^2y(t)/dt^2 + 13dy(t)/dt + 4y(t) = din(t)/dt + 3in(t)$$

- (e) Find the transfer function for this circuit.
- (f) Write a Matlab script to express the transfer function in symbolic form and from this find the poles of the system.
- (g) Write a Matlab script to find the state space realization from the transfer function.
- (h) Write a Matlab script to find the total response when $x(0) = [-1, 2]'$ and $in(t) = \exp(-3) \cos(5t) u(t)$.